

## HW2

**30 Points**

Group # ?????			
Name	Last Name	% Effort	Lab Section A - 2:00-3:15pm / B- 3:30:4:45pm / C- 5:00-6:15pm
?	?	?	?
?	?	?	?
?	?	?	?


**-2 pt per missing “Group #”, “Name”, “Last Name”, “% Effort”, “Lab Section”**

Grading:

- Will randomly pick a subset of the questions and scale the overall score to 30 points.
- 5pts per day late penalty
- 4pts penalty per skipped question
- **Show your work in order to receive full credit. If you write the final result only (without showing how you derived it), then you will receive partial credit even if the answer is correct.**



### Problem 2 (15pts):

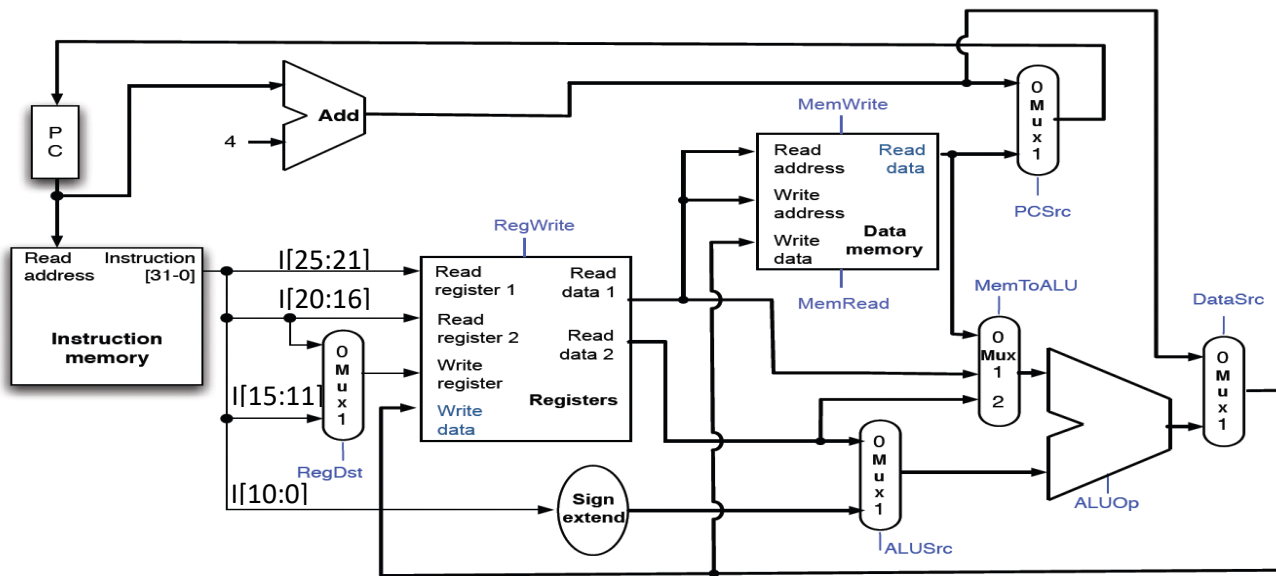

**Part (a)** You will implement the “ece369” instruction that will complete the process given below in one cycle.

```
ece369 $t0 $t1    # PC = Memory[GPR[t0]]
                  # Memory[GPR[t1]] = GPR[t1] + 4
                  # GPR refers to general purpose register (register file)
```

opcode I[31:26]	rs I[25:21]	rt I[20:16]	rd I[15:11]	imm I[10:0]
64	t0	t1		

**You are allowed** to make changes in the “ece369” specification for utilizing the unused fields (rd and imm fields) in the instruction. Three of the instruction fields are filled for you. “opcode” is the integer value 64 for the “ece369” operation and, two source registers use “rs” and “rt” fields of “ece369 \$t0 \$t1” instruction. When applicable, **indicate your changes to the unused fields above with a label or value (in decimal).**

**You are allowed** to modify the datapath with new datapath components, wires, control signals, etc. **Show your modification(s) on the datapath given above.** While we are primarily concerned about correctness, full points will be rewarded to **solution with minimal hardware and latency overhead.** Table in the next page shows the latency for each datapath component. Adding a new input line to a mux introduces additional 1ns latency. Your modification(s) should not affect the functionality of the other types of instructions.


**Finally, in the table below, indicate the value of each control signal in order to realize the “ece369” instruction. Use X for don’t care when needed. ALUOp can be one of the following operations: add, sub, mul, sll, and srl. Assume that we can read and write the memory in the same cycle (like the register file, but this is likely not efficient to do in a real machine).**

[illegible]

**Part (b)** Given the functional unit latencies, what is the **minimum cycle time** based on the “ece369” instruction? Assume PC has no delay. Show your critical path delay analysis using a graph where each node represents a function unit and each edge represents the data flow from one node to another. **Indicate the function units that are on the critical path.** Show your work to get credit.

Func.Unit	Delay
Memory Read	5ns
Memory Write	2ns
ALU	3ns
Register Read	2ns
Register Write	4ns
3:1 Mux	2ns
2:1 Mux	1ns
Adder	3ns
sign extension	3ns

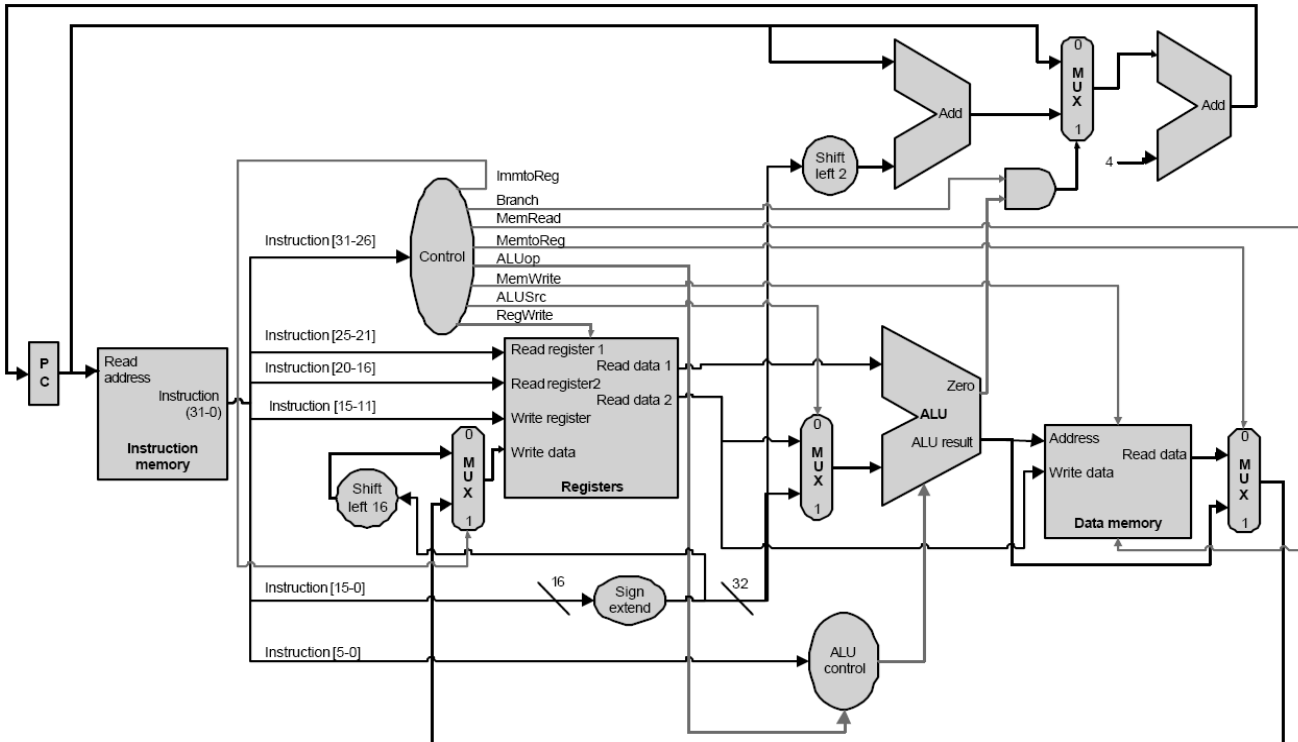**Problem 3. (15pts):** Some of the following instructions can *not* be carried out in the provided datapath. Explain why in the space after each instruction that can't be implemented.



1) `add rd, rs, rt`

0	rs	rt	rd	0	0x20
6	5	5	5	5	6

Can be implemented

2) `lw rt, offset(rs)`

0x23	rs	rt	offset
6	5	5	16


Cannot be implemented because this instruction requires `rt` to be written to. At the moment, `rt` cannot be written to since `instruction[20-16]` has no path to the write register input.

3) `j target`

2	target
6	26


Cannot be implemented because `instruction[25-0]` has no path to any of the program counter logic

4) lui rt, imm

 

Cannot be implemented because currently only register rd (instruction[15-11]) has a path to write register input. Thus, only rd can be written to.

5) bne rs, rt, label

 

Cannot be implemented because currently, to branch, the only option is if the zero output of the ALU is a 1 (indicating that the two ALU inputs are equal). This is equivalent to a beq operation. Thus, bne is not supported

**Problem 4: (15 points)**

Your single-cycle processor seems to be executing random instructions. You need to find out why. On the next page is a picture of your datapath (note that this is somewhat different from the datapath used in class) and the control table is below. You suspect that the controller is broken. You may assume that the datapath modules (e.g., the ALU, etc.) work correctly.

Opcode	PCSrc	Bequal	RegDst	RegWr	ExtOp	ALUSrc	ALUCtr	MemWr	MemToReg
addu	0	0	0	1	1	X	0	0	0
subu	0	0	1	1	X	0	0	0	0
beq	0	1	X	0	X	0	3	0	X
jr	2	1	X	0	X	X	X	0	X

You may assume the following are correct:

- The register file and memory both write on the rising clock edge when their respective control signals, RegWr and MemWr, are asserted.
- The extender will zero extend if the ExtOp bit is 0 and sign extend when the ExtOp bit is 1.
- The data memory reads asynchronously but has synchronous writes.
- The “=0?” module will output 1 if all the input bits are 0, and will output 0 otherwise.

The ALUCtr encoding is as follows:


Control bits	Operation
0	add
1	sub
2	or
3	xor

For the following stream of instructions, what does your broken processor actually do? Here are some possible answers.

- **Functions correctly**
- **Incorrect functionality:** Indicate the control signals causing this error, and if it implements a different instruction then specify that instruction including the type of operation and registers used (operation, rs, rt, rd)
- **Functions correctly only under certain circumstance(s):** Specify the circumstance

If there is more than one possibility, list all of them. For simplicity, we have used the actual register numbers rather than names.

## Datapath

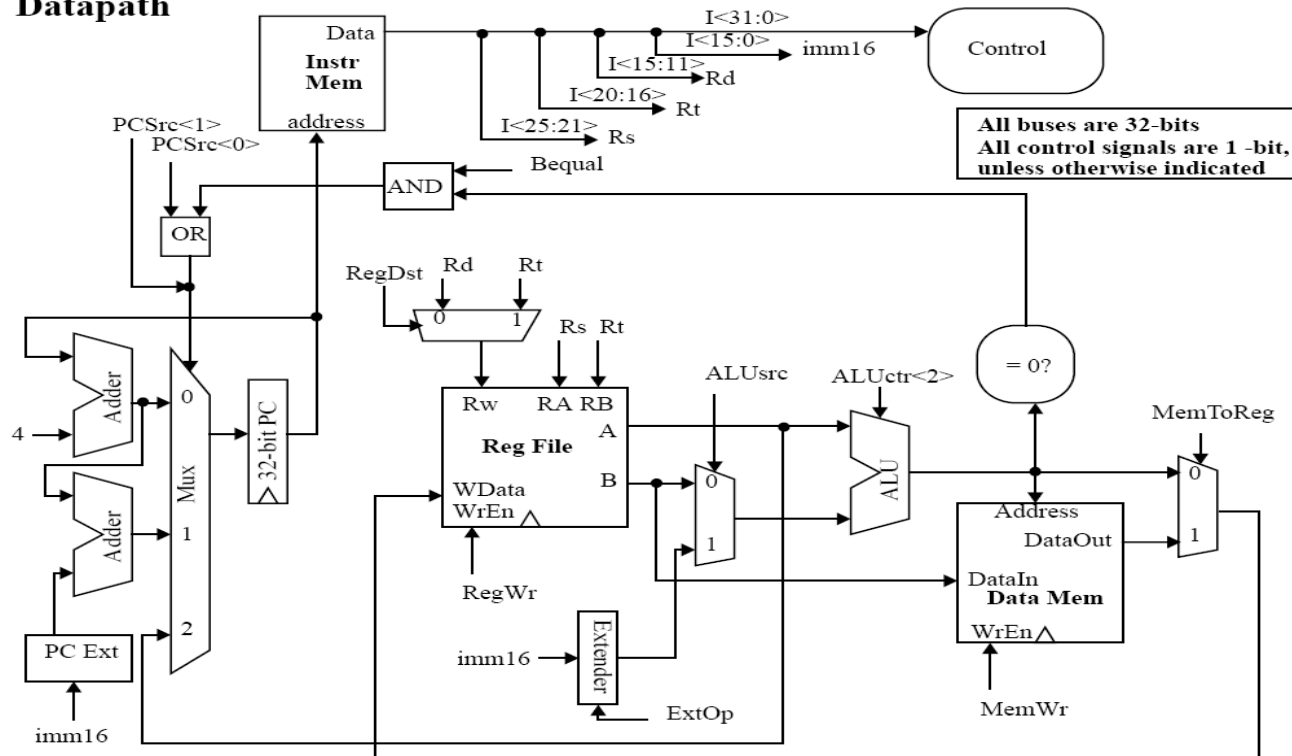


Instruction	Possible behavior(s) and Justification to get credit
<b>subu \$4, \$5, \$6</b>	Incorrect Functionality: $RegDst$ should be 1 to write to $rd$ since $subu$ is an R-type instruction. Additionally, $ALUctr$ should be 1 to indicate subtraction instead of 0 for addition. This would in practice simulate a fictitious operation that would function like $addu $4, $5, $6$
<b>addu \$4, \$5, \$6</b>	Functions correctly under certain circumstances: $ALUSrc$ is listed as "X" (don't care), if $ALUSrc$ is 0, $addu$ functions as intended; however, if $ALUSrc$ is 1, $addu$ will try to save $rs$ plus the sign extended immediate into register $rd$ .
<b>beq \$11, \$12, 24</b>	Functions correctly
<b>jr \$9</b>	Functions correctly



### Problem 5 (15pts):

Single Cycle Datapath:

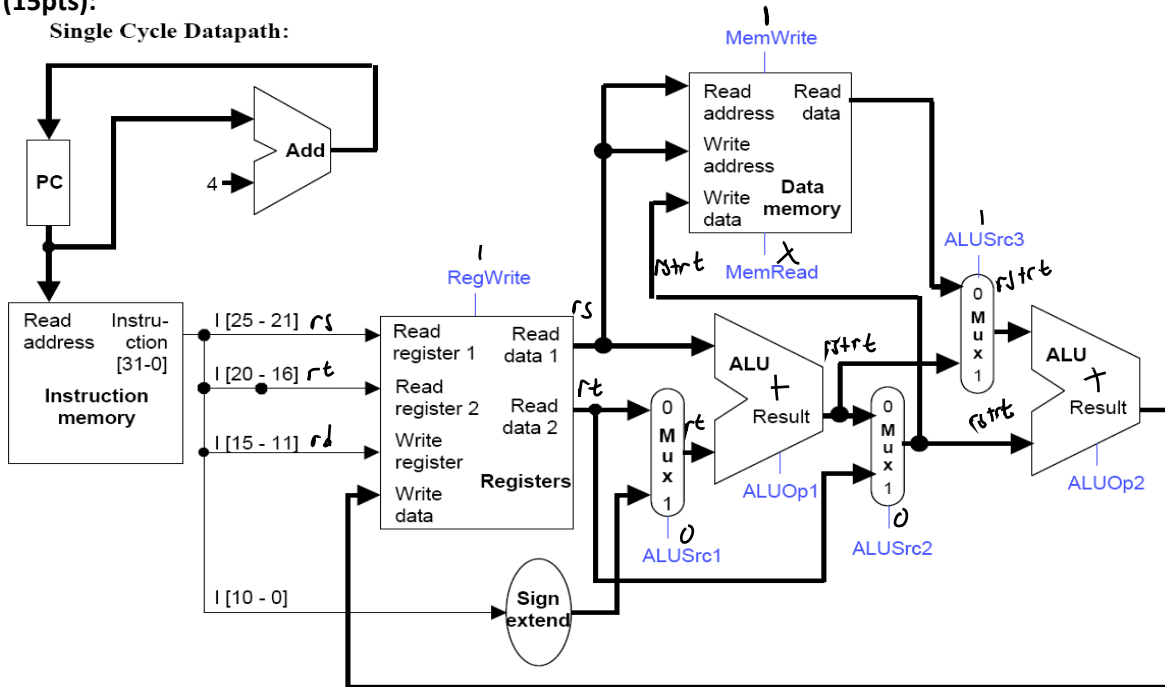

Field	op	rs	rt	rd	imm
Bits	31-26	25-21	20-16	15-11	10-0

**Part (a)** Assume that for the single cycle datapath shown above all instructions use the same format, but not all instructions use all of the fields. Assume that each unused field is set to 0. ALU operation (ALUOp) can be one of the following operations: add, sub, mul, sll, and srl. Specify how the control signals should be set for correct operation of the “mov” instruction. Use X for don’t care. You are not allowed to modify the datapath.


mov rs, rt, rd # Memory[R[rs]] = R[rs] + R[rt]; R[rd] = 2\*R[rs] + 2\*R[rt]

Instr	RegWrite	ALUSrc1	ALUOp1	ALUSrc2	ALUSrc3	ALUOp2	MemRead	MemWrite
mov	1	0	add	0	1	add	X	1

**Part (b)** Given the functional unit latencies, what is the **minimum CPI** and **minimum cycle time** based on the “mov” instruction? Assume PC has no delay. Show your critical path delay analysis using a graph where each node represents a function unit and each edge represents the data flow from one node to another. Show your work to get credit.


mov rs, rt, rd #Memory[R[rs]] = R[rs] + R[rt]; R[rd] = 2\*R[rs] + 2\*R[rt]

Func.Unit	Delay
Inst. Memory	5ns
Data Memory (Write)	9ns
Data Memory (Read)	6ns
ALU	4ns
Register (Read)	1ns
Register (Write)	4ns
Mux	1ns
Add	2ns
SignExtend	2ns

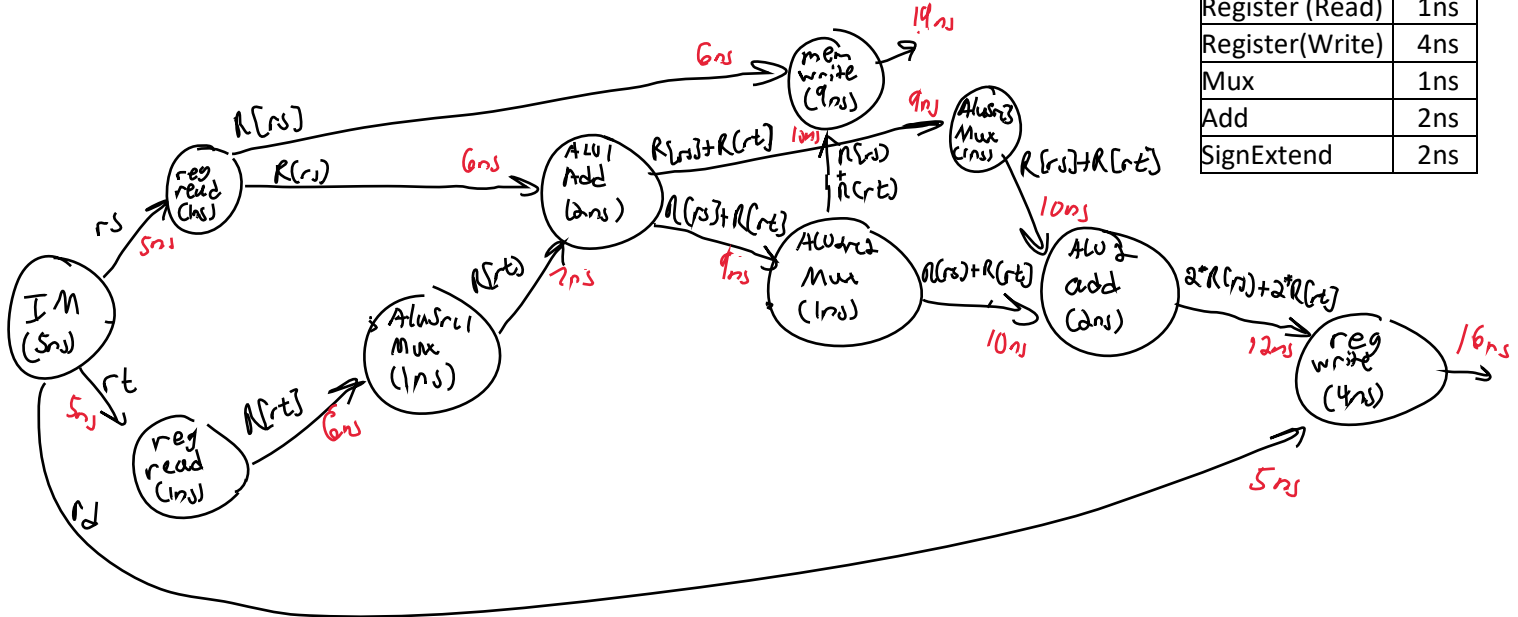

minimum cycle time is 19 ns

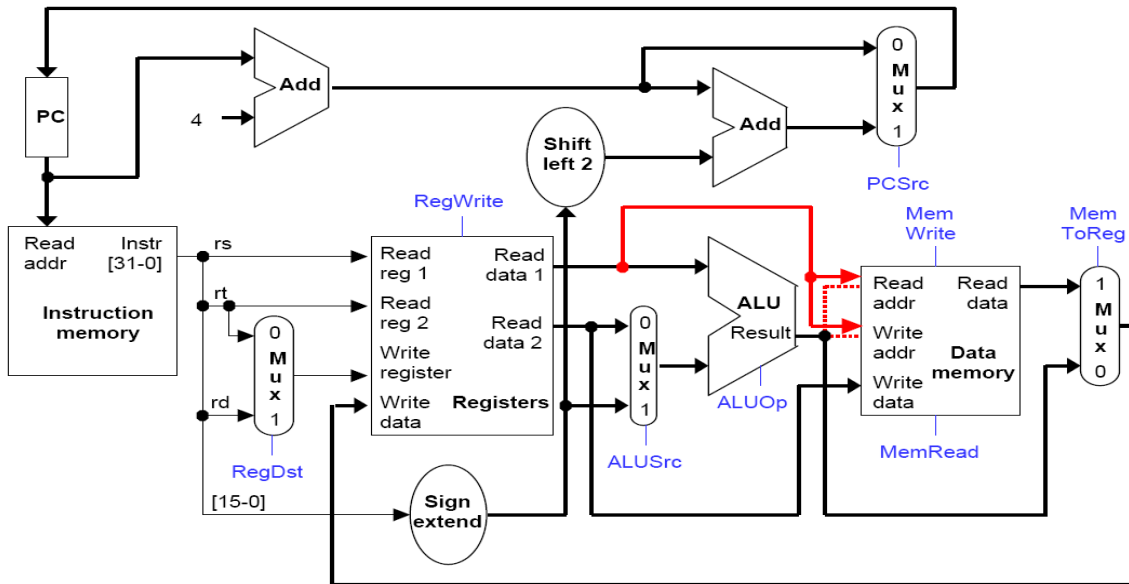minimum CPI is 1 cycle since mov only takes one cycle



### Problem 6 (15pts):

Your teammate proposes to simplify the MIPS instruction set architecture for the competition phase of the project by removing the support for original lw and sw instructions (all memory accesses ) and replacing them with ones that do not contain a constant offset. In the simplified instruction set, new loads and stores will have the following general forms:

lw rt, rs # GPR[rt] = Memory[GPR[rs]]

sw rt, rs # Memory[GPR[rs]] = GPR[rt]

Your teammate modifies the datapath to support the new lw and sw instructions as shown above. The dotted red lines show wires that are removed from the original design and solid red lines with arrow indicate the new wires. Assume that memory accesses (reads/writes) and ALU each take 2ns, register file and adders each take 1ns, and all other components have negligible delay. Considering all instruction types, your teammate claims that minimum cycle time will be shorter than the original datapath because lw/sw instructions no longer need the ALU for address calculation.

How much time is saved in ns compared to the minimum cycle time of the original datapath executing the standard R-type, I-type MIPS instructions? Your teammate claims that due to reduction in cycle time for this datapath, the clock rate will be faster, therefore revised datapath will execute programs faster compared to the original datapath. True/False. Justify your answer.